

# **INTENSIVE TRAINING PROGRAM 2025 REPORT**

## **GROUP 4 – BAYMAX**

### **VENDING MACHINE'S SPECIFICATION REPORT**

*10/03/2025 – 13/03/2025*

CONTENT

- I. General purpose ..... 1
  - 1. Overview ..... 1
  - 2. Functional behavior ..... 1
- II. Top module ..... 2
- III. Submodule ..... 6
  - 1. FSM ..... 6
  - 2. Output Handler ..... 15

## I. General purpose

### 1. Overview

Design Description					
<p>Design a vending machine capable of accepting multiple deposits of three denominations: 5, 10, and 20. When a user selects a product, the machine will check the total amount deposited:</p> <ul style="list-style-type: none"><li>• If the deposited amount is greater than or equal to the product price, the machine will dispense the product and return any change (if applicable).</li><li>• If insufficient, the machine will prompt the user to add more money or cancel the transaction.</li><li>• The user can cancel the transaction any time after depositing money, and the machine will refund the full amount.</li></ul>					
No.	Parameter description	Min	Typ	Max	Units
1.	Process				
2.	Voltage				V
3.	Temperature				°C
4.	Power Dissipation				mW
5.	Die Area				um <sup>2</sup>
6.	Clock frequency				GHz

Table 1: Specification of Vending Machine

### 2. Functional behavior

The vending machine is designed to dispense items based on user selection and payment. It operates using a finite state machine (FSM) and interfaces with input and output signals for control and monitoring.

#### Item Selection and Payment:

- The user presses start to begin.
- The user selects an item using item\_in.
- The user inserts money (money signal).
- The system waits until done\_money = 1 before moving forward.

#### Comparison:

- If the inserted money is sufficient, the system proceeds to dispense the item.
- If the money is insufficient, the transaction is canceled.

#### Dispensing Items and Returning Change:


- Once sufficient money is received, item\_out is activated to dispense the selected item.

- If excess money is inserted, change is calculated and returned.

#### **Cancellation Handling:**

- If cancel = 1, the transaction is aborted.
- If money was inserted, the system returns the money before resetting.

## **II. Top module**

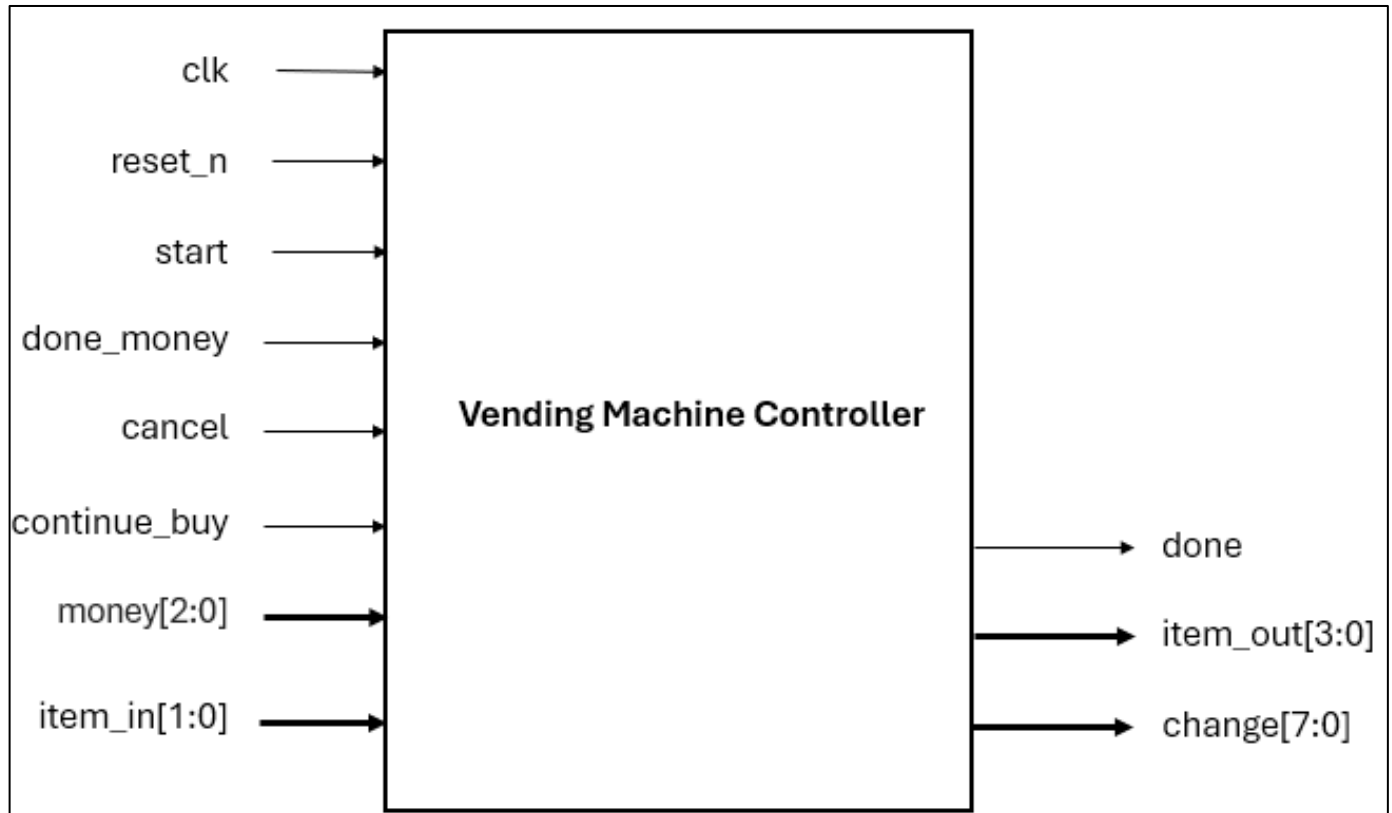

*Figure 1: Vending Machine Controller Block Diagram*

signal name	width	default value	direction	description
clk	1	0	input	clock
reset_n	1	1	input	Reset active low (asynchronous)
start	1	0	input	Start signal to begin item selection.
done_money	1	0	input	Confirmation signal indicating sufficient money has been inserted.
cancel	1	0	input	Signal to cancel the transaction and refund money.
continue_buy	1	0	input	Continue to buy the next item when returned change
money	3	000	input	Denomination of money inserted by the user.
item_in	2	00	input	Code of the item chosen by the user.
done	1	0	output	Indicating the transaction was completed successfully
item_out	4	0000	output	Code representing the dispensed item.
change	8	0000_0000	output	Amount of change to be returned to the user.

Table 2: The signal pins of Vending Machine Controller block

Signal	Value	Action/ Meaning
clk	1'b0 / 1'b1	Signal clock
reset_n	1'b0	Reset the circuit, reload default values for variables
	1'b1	The circuit operates normally
start	1'b0	In wait mode
	1'b1	Start transaction
done_money	1'b0	After inserting money, continue inserting more
	1'b1	After inserting money, stop adding more and proceed to the next step
cancel	1'b0	Continue the transaction process.
	1'b1	Stop the transaction, return the inserted money (if any), and revert to wait mode
continue_buy	1'b0	After returning the change, stop and do not proceed with the transaction (must remain in standby mode until signal start = 1 to begin a new transaction)
	1'b1	After returning the change, continue the transaction at the item selection step
money	3'b001	Corresponding to the inserted denomination of 5
	3'b010	Corresponding to the inserted denomination of 10
	3'b100	Corresponding to the inserted denomination of 20
	else	The denomination is not accepted, and no additional money is inserted into the machine
item_in	2'b00	Corresponding to selecting item 1

	2'b01	Corresponding to selecting item 2
	2'b10	Corresponding to selecting item 3
	2'b11	Corresponding to selecting item 4
done	1'b0	No item was purchased
	1'b1	One item was purchased
item_out	4'b0000	No item was purchased
	4'b1000	The first item was purchased
	4'b0100	The second item was purchased
	4'b0010	The third item was purchased
	4'b0001	The fourth item was purchased
	else	This output should not appear
change	[8'b0000_0000 :8'b1111_1111]	Total change amount

Table 3: The meaning of the signal for each corresponding value of Vending Machine Controller block

### III. Submodule

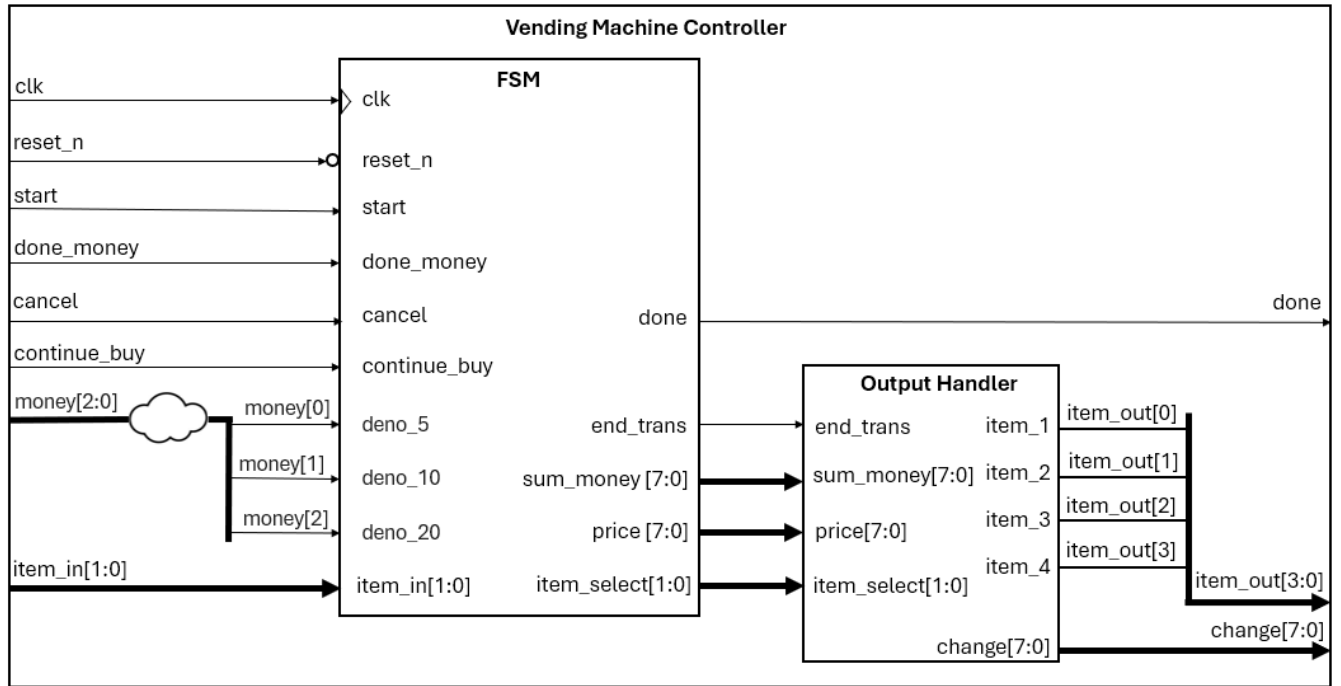


Figure 2: Submodules of Vending Machine Controller block

#### 1. FSM

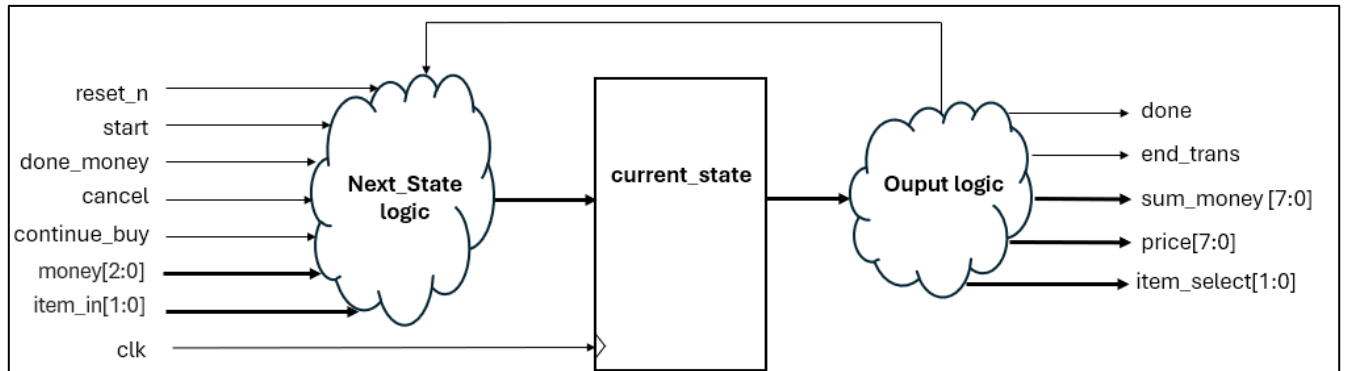


Figure 3: FSM's block diagram



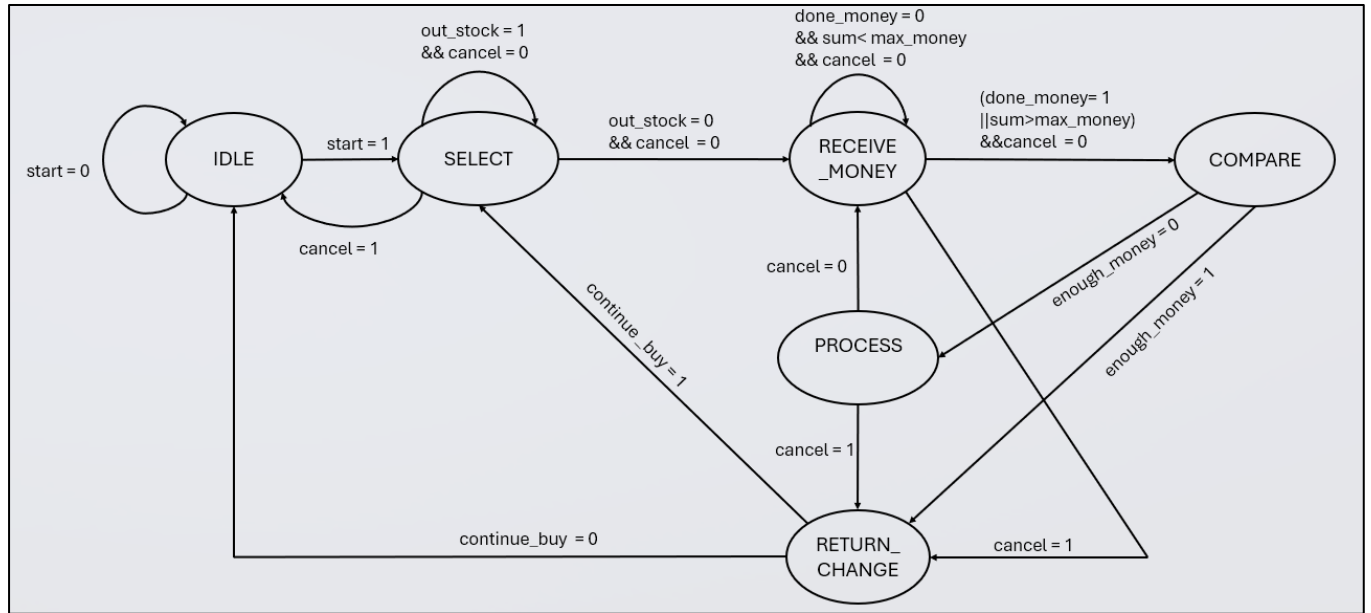


Figure 4: FSM states and transitions

In addition to the input values, the diagram also shows several other signals and variables. `out_stock` will be set to 1 when the selected item is out of stock. `sum` will be a variable that holds the total amount of money inserted into the machine, `max_money` is a threshold for the amount of money inserted (which can be set to 40), and `enough_money` will be set to 1 when the total amount of money is greater than or equal to the price of the item.

current_state	Signal / Condition			next_state
IDLE	start = 1'b0			IDLE
	start = 1'b0			SELECT
SELECT	cancel = 1'b1	out_stock = 1'bx		IDLE
	cancel = 1'b0	out_stock = 1'b0		RECEIVE_MONEY
	cancel = 1'b0	out_stock = 1'b1		SELECT
RECEIVE_MONEY	cancel = 1'b1	done_money = 1'b x	sum > max_money = 1'bx	RETURN_CHANGE
	cancel = 1'b0	done_money = 1'b 0	sum > max_money = 1'b0	RECEIVE_MONEY
	cancel = 1'b0	done_money = 1'b 0	sum > max_money = 1'b1	COMPARE

	cancel = 1'b0	done_money = 1'b 1	sum > max_money = 1'b0	COMPARE
	cancel = 1'b0	done_money = 1'b 1	sum > max_money = 1'b1	COMPARE
COMPARE	enough_money = 0			PROCESS
	enough_money = 1			RETURN_CHANGE
PROCESS	cancel = 0			RECEIVE_MONEY
	cancel = 1			RETURN_CHANGE
RETURN_CHANGE	continue_buy = 0			IDLE
	continue_buy = 1			SELECT

Table 4: Truth table of FSM

No.	state	Output	
1	IDLE	done	1'b0
		end_trans	1'b0
		sum_money	8'b0
		price	8'b0
		item_select	2'b0
2	SELECT	done	1'b0
		end_trans	1'b0
		sum_money	8'b0
		price	8'b0
		item_select	2'b0

3	RECEIVE_MONEY	done	1'b0
		end_trans	1'b0
		sum_money	8'b0
		price	8'b0
		item_select	2'b0
4	COMPARE	done	1'b0
		end_trans	1'b0
		sum_money	8'b0
		price	8'b0
		item_select	2'b0
5	PROCESS	done	1'b0
		end_trans	1'b0
		sum_money	8'b0
		price	8'b0
		item_select	2'b0
6	RETURN_CHANGE	done	= 1'b1 if buy successful 1 item, else = 1'b0
		end_trans	1'b1
		sum_money	Value of sum_money
		price	Price of the selected item
		item_select	Selected item

Table 5: The output in each state

Inside the FSM, we will define an internal structure to store information about the products, including price and remaining quantity. The values will be declared as shown in the table below. Upon reset, we will return the values to those shown in the table.

Item	Default price	Default quantity
00	3	1
01	12	2
10	25	3
11	45	4

Signal	Width	Default value	Direction	Description
clk	1	0	input	Clock
reset_n	1	1	input	Reset active low (asynchronous) (*)
start	1	0	input	Start signal to begin item selection.
done_money	1	0	input	Confirmation signal indicating sufficient money has been inserted.
cancel	1	0	input	Signal to cancel the transaction and refund money.
continue_buy	1	0	input	Continue to buy the next item
deno_5	1	0	input	Is the denomination 5?
deno_10	1	0	input	Is the denomination 10?
deno_20	1	0	input	Is the denomination 20?
item_in	2	0	input	Code of the item chosen by the user.
done	1	0	output	Indicating the transaction was completed successfully

end_trans	1	0	output	End a transaction
sum_money	8	0	output	Total of money
price	8	0	output	Price of the item that has been selected
item_select	2	0	output	The item has been selected

Table 6: The signal pins of block Top design

Signal	Value	Action/Meaning
clk	1'b0 / 1'b1	Signal clock
reset_n	1'b0	The circuit resets and reloads the default values for the variables.
	1'b1	The circuit operates normally.
start	1'b0	Stay at state IDLE
	1'b1	Transition to state SELECT
done_money	1'b0	If in the RECEIVE-MONEY state, remain in the same state at the next clock cycle
	1'b1	If in the RECEIVE-MONEY state, stop inserting money and transition to the next state.
cancel	1'b0	Maintain the transaction process
	1'b1	Stop the transaction and transition to the RETURN-CHANGE state at the next clock cycle
continue_buy	1'b0	In the RETURN-CHANGE state, the transaction will stop and transition to the IDLE state at the next clock cycle.
	1'b1	In the RETURN-CHANGE state, the transaction will continue and transition to the SELECT state at the next clock cycle.
deno_5	1'b0	Do not increase the total amount.
	1'b1	If state = RECEIVE-MONEY, increase the total amount by 5
deno_10	1'b0	Do not increase the total amount.

	1'b1	If state = RECEIVE-MONEY, increase the total amount by 10
deno_20	1'b0	Do not increase the total amount.
	1'b1	If state = RECEIVE-MONEY, increase the total amount by 20
item_in	2'b00	Corresponding to selecting item 1 (retrieve the price and quantity of the product)
	2'b01	Corresponding to selecting item 2 (retrieve the price and quantity of the product)
	2'b10	Corresponding to selecting item 3 (retrieve the price and quantity of the product)
	2'b11	Corresponding to selecting item 4 (retrieve the price and quantity of the product)
done	1'b0	No item was purchased or the transaction is not yet complete
	1'b1	One item has been purchased
end-trans	1'b0	The transaction is not yet complete.
	1'b1	The transaction has ended in the RETURN-CHANGE state
sum-money	[8'b0000_0000 :8'b1111_1111]	Total amount inserted.
price	[8'b0000_0000 :8'b1111_1111]	Price of the product.
item-select	2'b00	The first item has been selected.
	2'b01	The second item has been selected.
	2'b10	The third item has been selected.
	2'b11	The fourth item has been selected

Table 7: The meaning of the signal for each corresponding value of FSM design

This is the main state machine of the design. It consists of six states:

- IDLE – Initialization stage.
- SELECT – Selecting the type of goods.
- RECEIVE\_MONEY – Receiving money.

- COMPARE – Checking whether the inserted amount is sufficient for the purchase.
- PROCESS – Adding more money or finalizing the transaction.
- RETURN\_CHANGE – Returning the remaining balance.

Initially, the machine remains in the IDLE state until the start signal is activated, at which point it transitions to the SELECT state. In the SELECT state, the machine receives an item input to choose the desired product. If the quantity of the selected item is greater than zero, the machine transitions to the RECEIVE\_MONEY state. Money is inserted based on the money input, which corresponds to specific values:

- money = 100 → Adds 5
- money = 010 → Adds 10
- money = 001 → Adds 20

This process continues until either done\_money is activated or the total inserted amount exceeds max\_money, at which point the machine transitions to the COMPARE state. In the COMPARE state, the inserted money is compared with the price of the selected product: If the amount is insufficient, the machine transitions to the PROCESS state. Depending on the cancel input, two scenarios arise: if cancel = 0, the machine returns to RECEIVE\_MONEY to accept additional money. if cancel = 1, the machine moves to RETURN\_CHANGE to fully refund the inserted amount. If the inserted money is sufficient for the purchase, the machine transitions to RETURN\_CHANGE to return any excess money. Additionally, the cancel = 1 signal is also valid in the RECEIVE\_MONEY state to stop and refund the money, or in the SELECT state to cancel the transaction and return to IDLE. When the refunded amount is not equal to zero, the end\_trans output signal is activated.

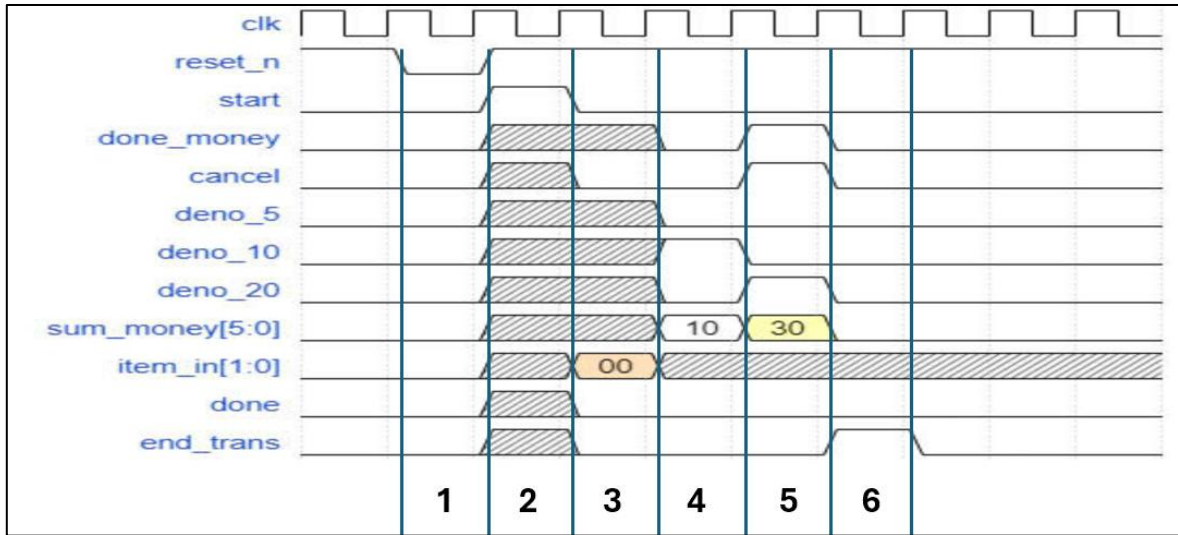


Figure 5: Timing Chart for testcase 1

The testcase represents the steps: 1. reset -> 2. start -> 3. select item 00 -> 4. insert 10 (sum = 10) -> 5. insert 20 (sum = 30) and cancel -> 6. entrans = 1 and done = 0 (end the transaction but don't buy successfully)

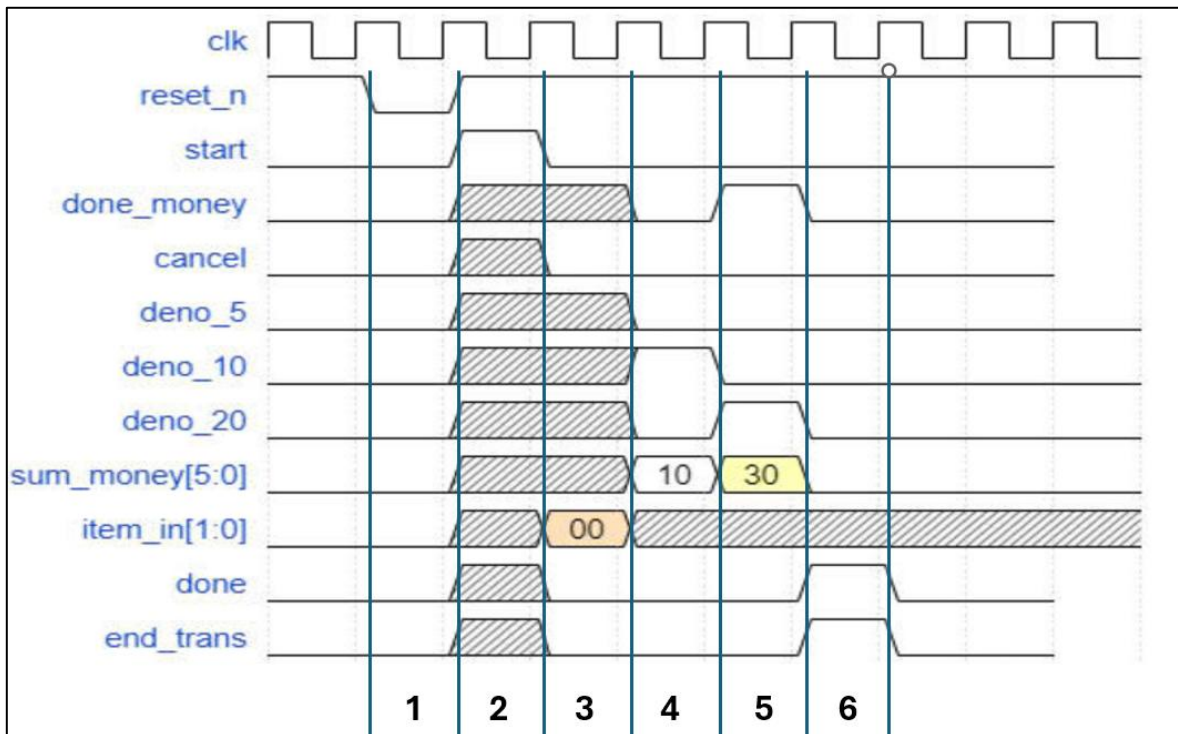


Figure 6: Timing Chart for testcase 2

The testcase represents the steps: 1. reset -> 2. start -> 3. select item 00 -> 4. insert 10 (sum = 10) -> 5. insert 20 (sum = 30) -> 6. entrans = 1 and done = 1 (end the transaction and buy successfully)



## 2. Output Handler

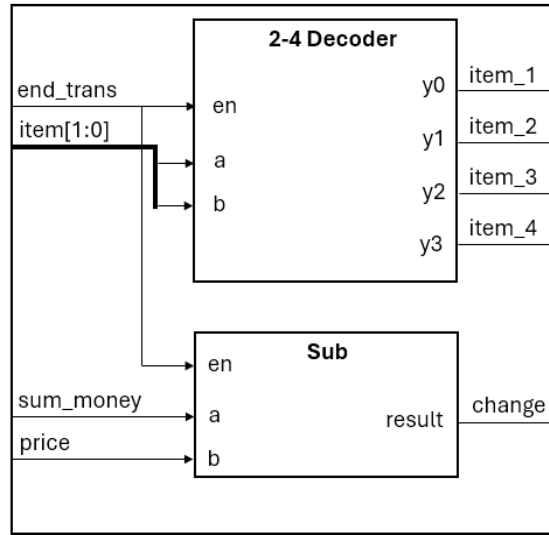


Figure 7: Output Handler's block diagram

signal	width	default value	direction	description
end_trans	1	0	input	end a transaction
sum_money	8	0	input	Represents the total amount of money received by the vending machine from the user.
price	8	0	input	price of the item that has been selected
item_select	2	0	input	the selected item
item_1	1	0	output	Indicates that item 1 has been dispensed.
item_2	1	0	output	Indicates that item 2 has been dispensed.
item_3	1	0	output	Indicates that item 3 has been dispensed.
item_4	1	0	output	Indicates that item 4 has been dispensed.
change	8	0	output	Represents the amount of change to be returned to the customer if the inserted money exceeds the item price.

Table 8: The pin signals of block Output\_Handler

Signal	Value	Action/ Meaning
end_trans	1'b0	All output = 0
	1'b1	The output ports can produce values.
sum_money	[8'b0000_0000 :8'b1111_1111]	Total amount inserted
price	[8'b0000_0000 :8'b1111_1111]	Price of the item
item_select	1'b00	Select item 1
	1'b01	Select item 2
	1'b10	Select item 3
	1'b11	Select item 4
item_1	1'b0	Item 1 was not successfully purchased
	1'b1	Item 1 was successfully purchased
item_2	1'b0	Item 2 was not successfully purchased
	1'b1	Item 2 was successfully purchased
item_3	1'b0	Item 3 was not successfully purchased
	1'b1	Item 3 was successfully purchased
item_4	1'b0	Item 4 was not successfully purchased
	1'b1	Item 4 was successfully purchased
change	[8'b0000_0000 :8'b1111_1111]	Total of change

Table 9: The meaning of the signal for each corresponding value

This block takes the item input to determine which of the four-item types (item\_0, item\_1, item\_2, item\_3) has been purchased. If an item is purchased, its corresponding value is set to 1, otherwise, it is 0. Additionally, the block outputs the change amount, which represents the remaining balance after deducting the purchase price. If the purchase is unsuccessful, the change output may be the entire inserted amount. When end\_trans = 0, the output value will always be 0.

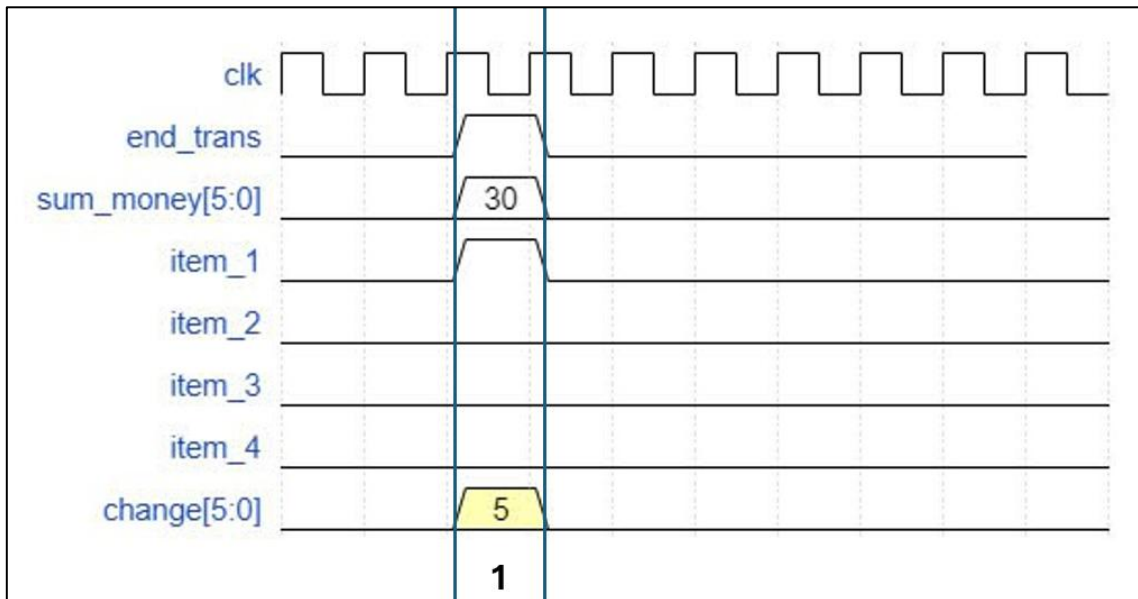


Figure 8: Timing Chart for testcase 3

The total amount is 30, and the product worth 25 is successfully purchased, leaving 5 as change.

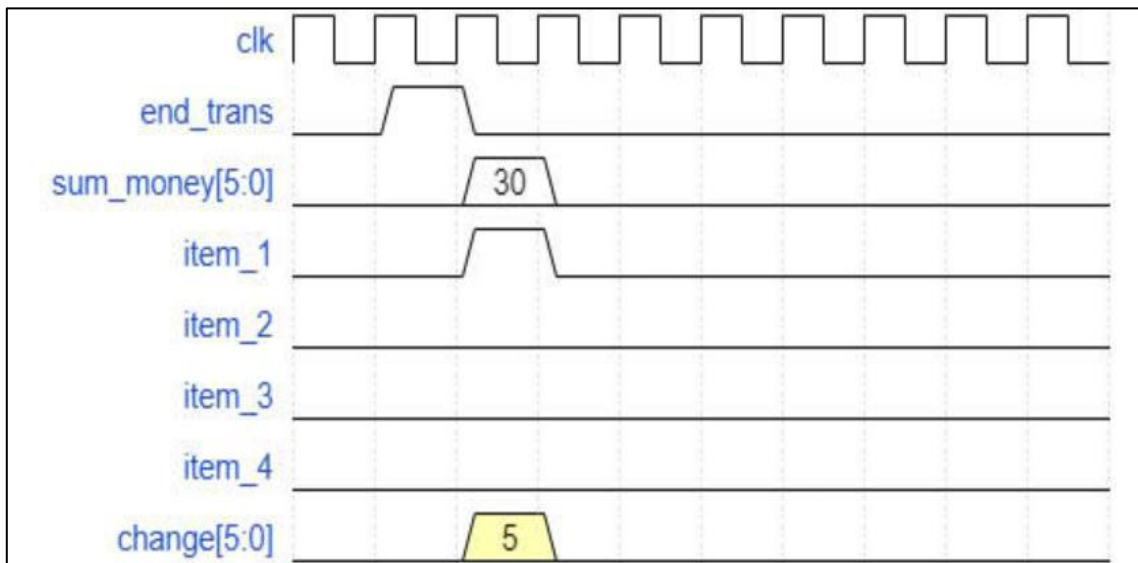


Figure 9: Timing Chart for testcase 4

The total amount is 30, and the product worth 35 is not successfully purchased, leaving 30.